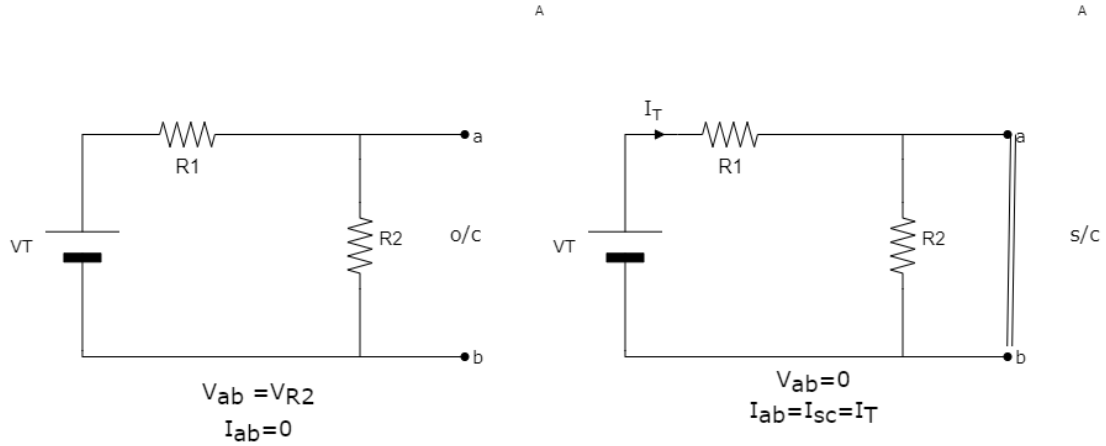


18: Open circuit and short circuit




For o/c there will be a voltage but no current.

For s/c there will be a current but no voltage.

EX.1: for the circuit shown below find:-

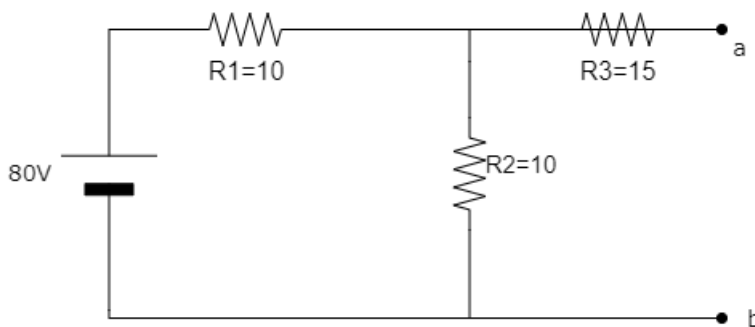
- 1-the open circuit voltage between points (a) and (b)
- 2-if the points (a) and (b) are short circuited, find the short circuit current.



Solution:-

1-when ab are open : $V_{ab} = V_{R2} = 80 * \frac{10}{10+10} = 40V$

2-when ab are short circuited, then

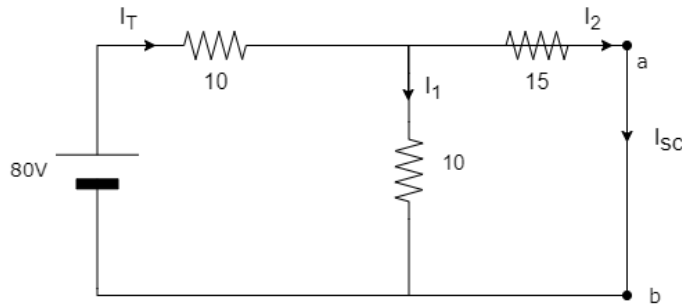

$$R_T = \frac{R_2 \cdot R_3}{R_2 + R_3} + R_1$$

$$= \frac{15 * 10}{15 + 10} + 10 = 16\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{80}{16} = 5A$$


$$I_{sc} = I_2 = I_T \frac{R_2}{R_2 + R_3} = 5 \frac{10}{10 + 15} = 2A$$

H.W: for the circuit shown below:-

1-find V_{AB} and I_2 .

2- -find V_{AB} and I_2 when points AB are open.

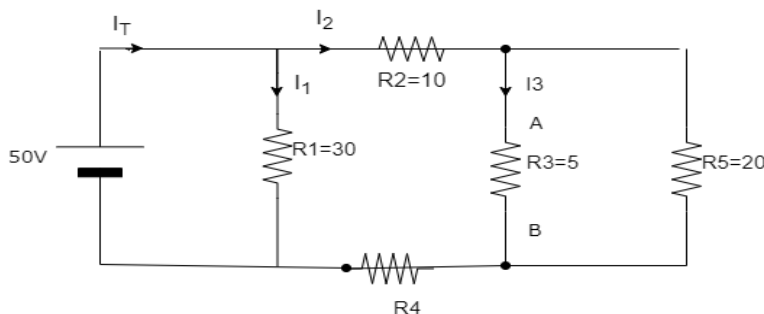3- -find V_{AB} and I_2 when points AB are shorted .




1- $V_{AB} = 5.88 V, I_2 = 1.47 A$

2- $V_{AB} = 20 V, I_2 = 1 A$



3- $V_{AB} = 0 V, I_2 = 1.666 A$

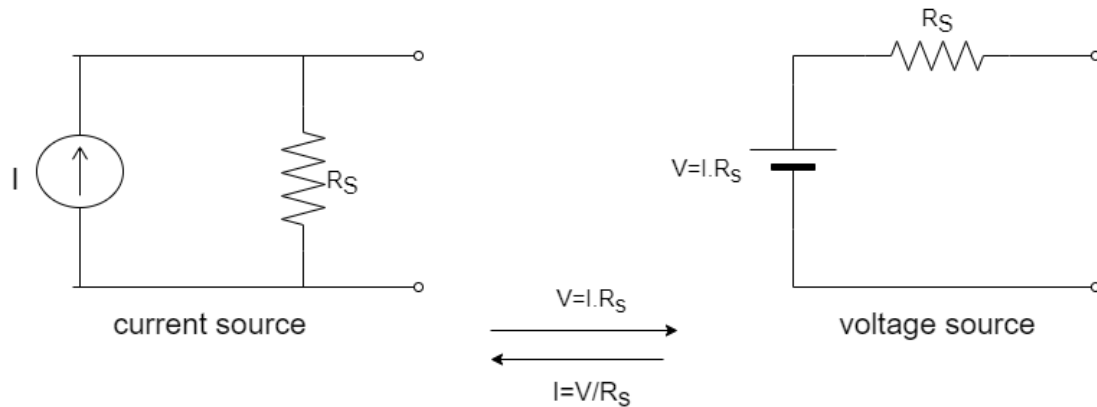19: conversion of energy sources



A current source having a current (I) and a source resistance (R_S) can be replaced by a voltage source with a voltage of ($I \cdot R_S$) and a source resistance (R_S)



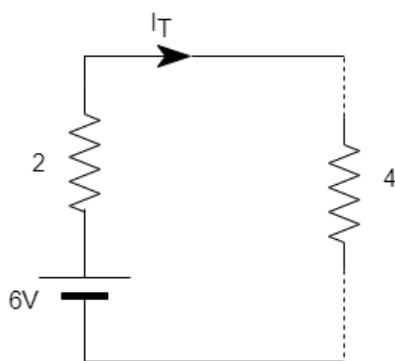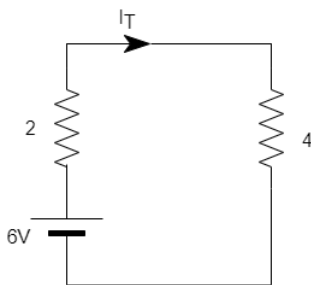EX: convert the voltage source shown below to a current source and calculate the current through the 4Ω load resistance for each source.



$$I_L = \frac{6V}{2+4} = 1A$$

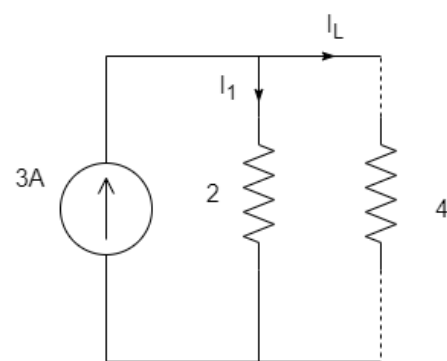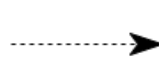

$$I_L = 3 * \frac{2}{2+4} = 1A$$



Example 4.6

28

★ Use source transformation to find v_o in the circuit in Fig 4.17.



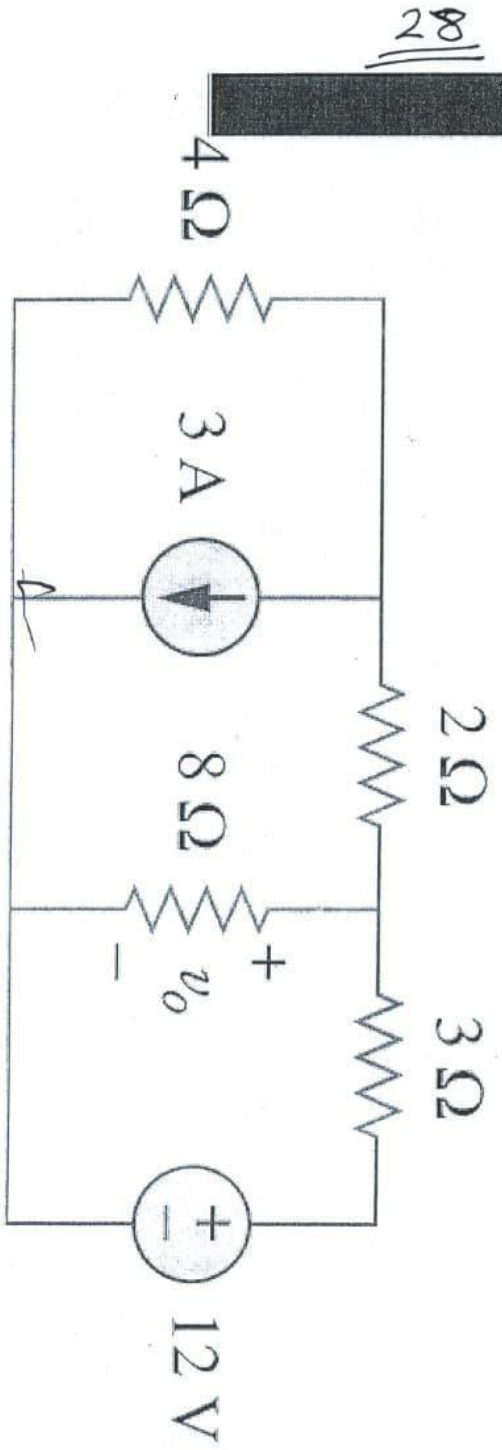
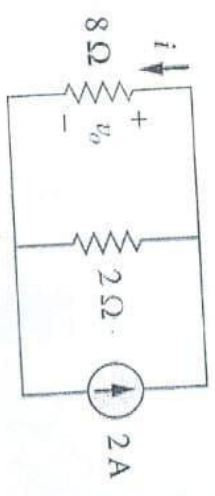


Fig (4.17)

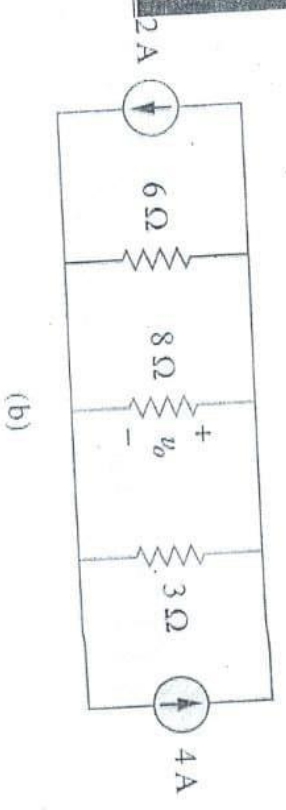

Example 4.6

Fig 4.18

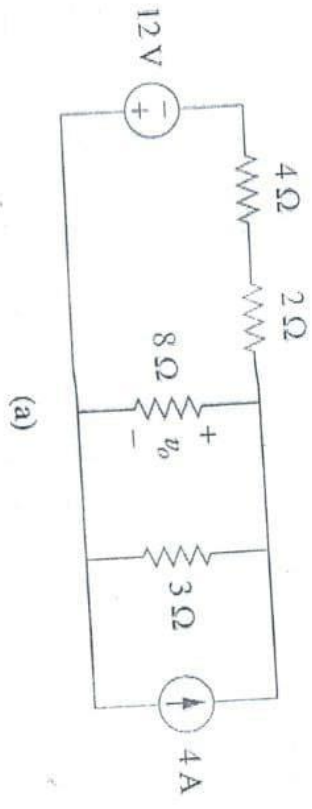

$$i = 2A \times \frac{2}{2+8} = 0.4A$$

$$\therefore V_o = 0.4 \times 8 = 3.2V$$

29



Example 4.6

we use current division in Fig.4.18(c) to get

$$i = \frac{2}{2+8}(2) = 0.4A$$

and

$$v_o = 8i = 8(0.4) = 3.2V$$

|||