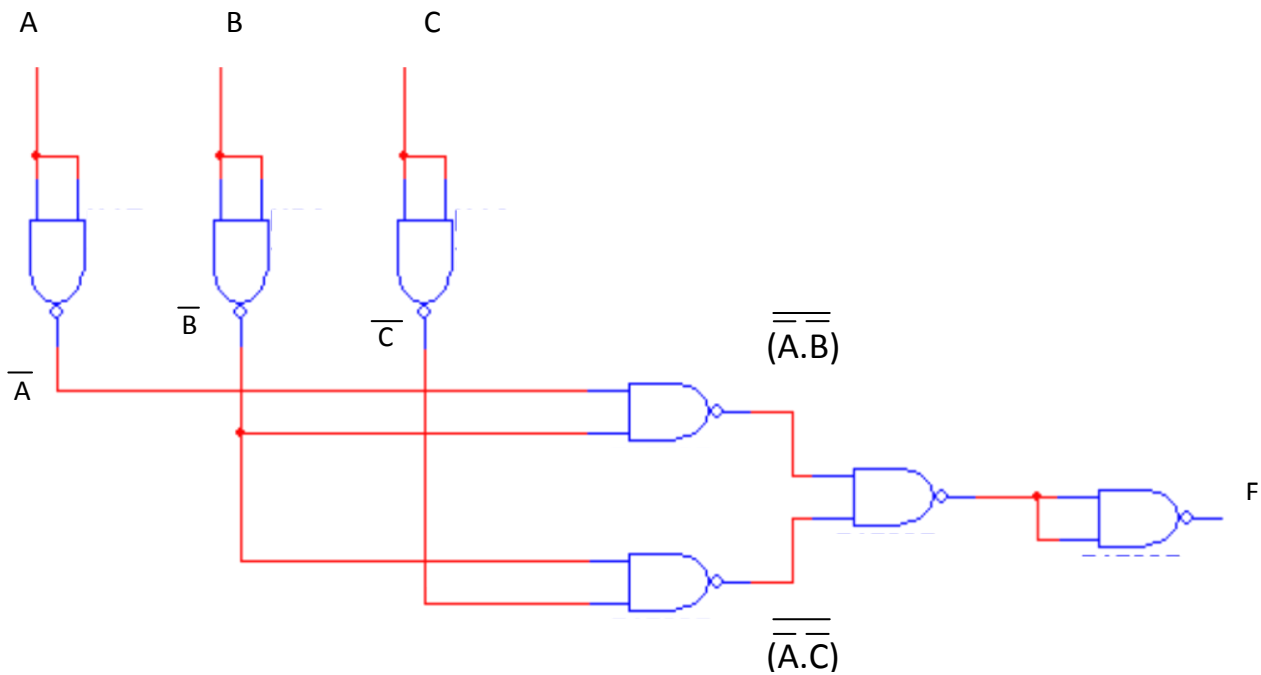


**Example 2 /** Implement the following expression using **NAND gate** only ?

$$F = (A+B)(B+C)$$

sol/

$$F = \overline{\overline{(A+B)} \overline{(B+C)}} = \overline{\overline{(A+B)} \overline{(B+C)}} = \overline{\overline{A \cdot B} + \overline{B \cdot C}} = \overline{\overline{A \cdot B}} \cdot \overline{\overline{B \cdot C}}$$



**Example 3/** Simplify the following expression, and implement using NOR gate only

$$A \overline{B} \overline{C} + A C + \overline{A} C \overline{D}$$

$$A(C + \overline{C} \overline{B}) + \overline{A} C \overline{D}$$

$$A(C + \overline{C})(C + \overline{B}) + \overline{A} C \overline{D}$$

$$A C + A \overline{B} + \overline{A} C \overline{D}$$

$$C(A + \overline{A} \overline{B}) + A \overline{B}$$

$$C(A + \overline{A})(A + \overline{D}) + A \overline{B}$$


$$C(A + \overline{D}) + A \overline{B}$$

$$A C + C \overline{D} + A \overline{B}$$

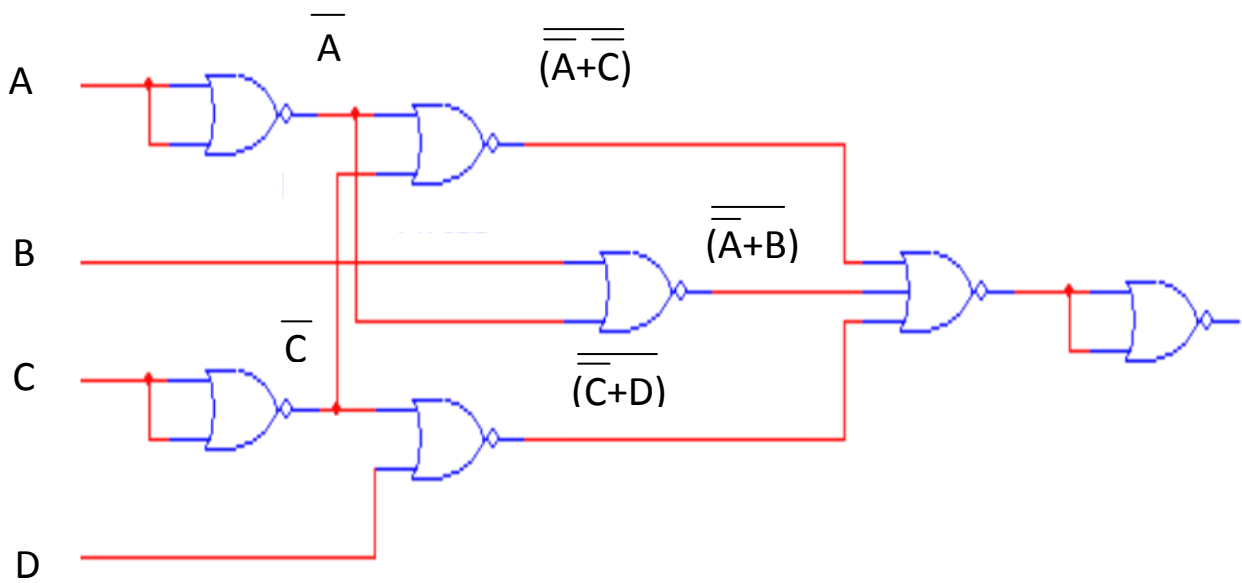**Example 4/** Implement this Boolean expression using NOR gate using de morgan's theorem

$$\overline{\overline{A}C + C\overline{D} + A\overline{B}} = \overline{\overline{A}C} \cdot \overline{C\overline{D}} \cdot \overline{A\overline{B}} = \overline{(\overline{A} + \overline{C})(\overline{C} + D)(\overline{A} + B)}$$

$$= \overline{\overline{(\overline{A} + \overline{C}) + (\overline{C} + D) + (\overline{A} + B)}}$$



## The XOR gate :-

The X-OR gates are formed by a combination of other gates .

The standard logic symbols is shown below :-



The logic expression is :-

$$x = A \oplus B$$

or

$$x = \bar{A}B + A\bar{B}$$

The truth table is :-

| I/P |   | O/P |
|-----|---|-----|
| A   | B | X   |
| 0   | 0 | 0   |
| 0   | 1 | 1   |
| 1   | 0 | 1   |
| 1   | 1 | 0   |

## The X-NOR gate :-

The X-NOR gates are formed by a combination of other gates .

The standard logic symbols is shown below :-



The logic expression is :-

$$x = \overline{A \oplus B}$$

or

$$x = \overline{A} \overline{B} + AB$$

The truth table is :-

| I/P |   | O/P |
|-----|---|-----|
| A   | B | X   |
| 0   | 0 | 1   |
| 0   | 1 | 0   |
| 1   | 0 | 0   |
| 1   | 1 | 1   |

## Applications of X-OR gate

The X-OR functions are very useful in systems require by error detection and correction codes . A parity bit is used for purpose of detecting errors during transmission of binary information . A parity bit is an extra bit included with a binary message to make a number of 1's either odd or even .

The circuit that generates the parity bit in the transmitter is called a **parity generator** which can be implemented using X-OR gate .

**Example / Design a 3- bit even parity generator circuit .**


$$\begin{aligned}
 P &= \bar{x} \bar{y} z + \bar{x} y \bar{z} + x \bar{y} \bar{z} + x y z \\
 &= \bar{x} (\bar{y} z + y \bar{z}) + x (\bar{y} \bar{z} + y z)
 \end{aligned}$$

$$\begin{array}{ccc}
 \text{M} & & \bar{\text{M}}
 \end{array}$$

$$M = y \oplus z$$


$$P = \bar{x} M + x \bar{M} = x \oplus M = x \oplus y \oplus z$$

| x | y | z | p |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

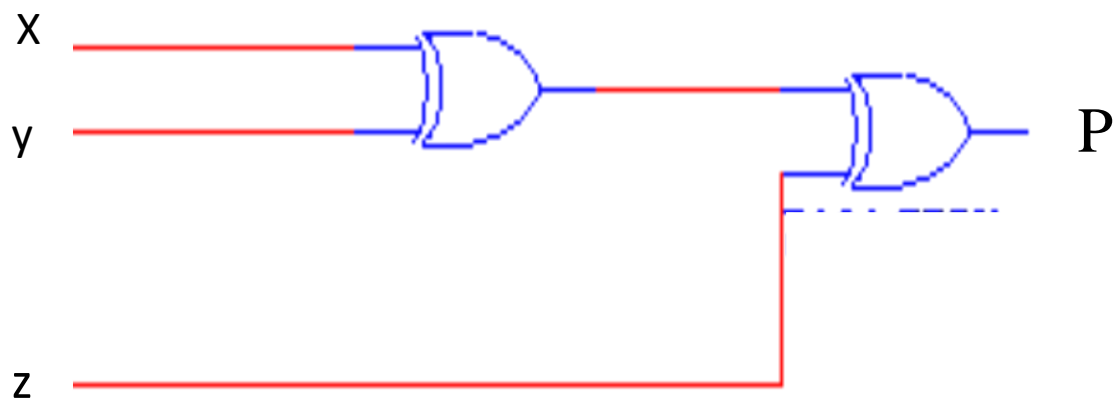
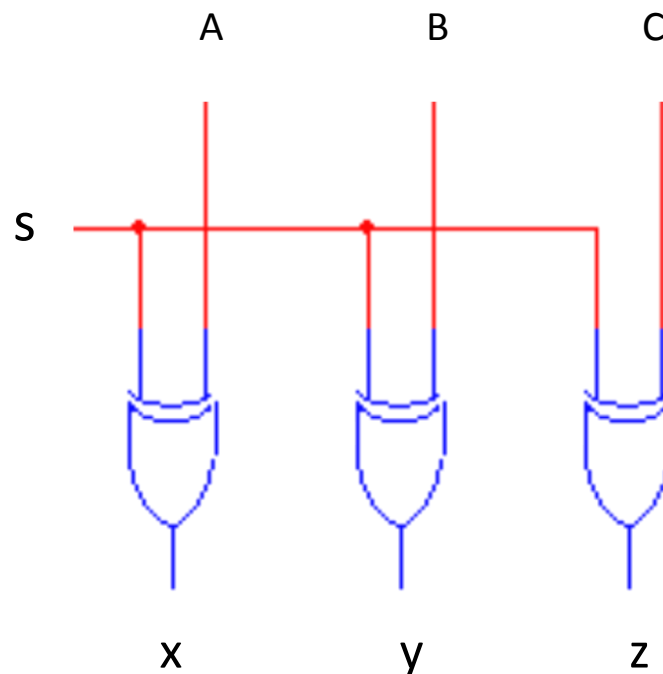
## Controlled inverter :-

The controlled inverter is used in the computer for subtraction :



The control signal (s)

\* IF  $s = 0$   $\longrightarrow$   $x = A, y = B, z = C$

\* IF  $s = 1$   $\longrightarrow$   $x = \overline{A}, y = \overline{B}, z = \overline{C}$

---

## Binary to Gray conversion :-


Gray code is unweighted code , not suited to arithmetic but useful for I/P , O/P devices such as shaft encoder, Analogue to digital convertor .

One of the main problem in binary number system is when going from one number to the next , more than one digit position may change at the same time.

But in Gray code every number differs from the preceding number by a single bit .

## How to convert from Binary to Gray :-

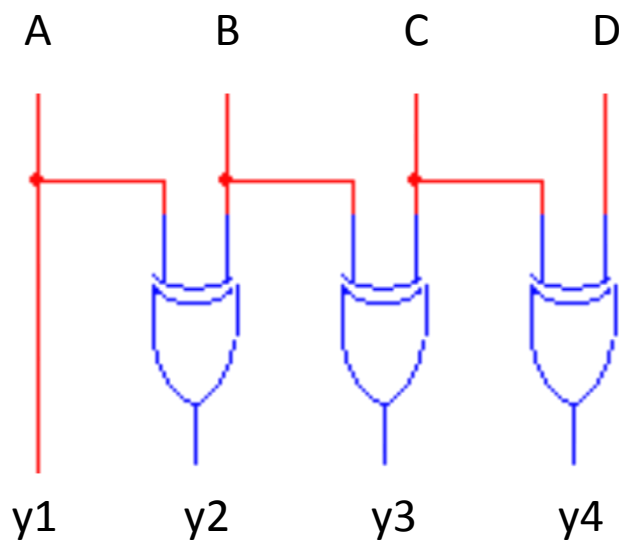
1. Gray digit is the same as the first Binary digit .
2. Add the list Binary to second Binary digit discard carries .




**Binary to Gray circuit**

Example / convert  $(1001)_2 \longrightarrow$  Gray

sol/

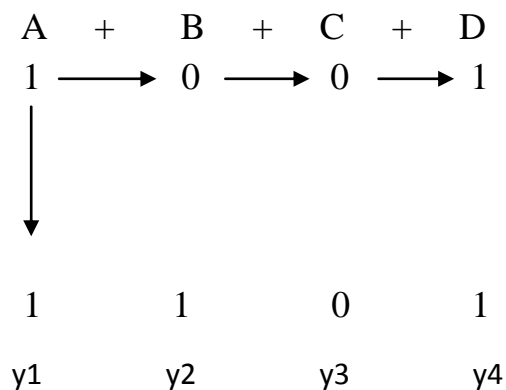

Gray to Binary conversion :-

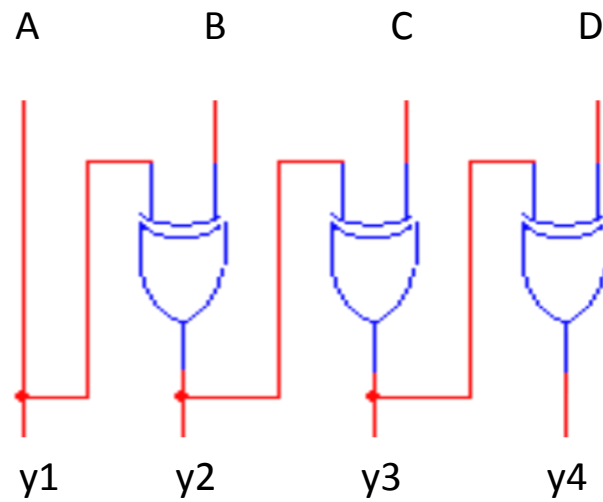

Example / convert (1101) Gray  $\longrightarrow$  Binary

sol/

