

DECODER


A Decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique O/P lines.

The Truth Table for a two - input (four - output) decoder is shown below :

The decoder consist of an ANDgate for each output , plus NOTgate to invert the Input


| a | b | 0 | 1 | 2 | 3 |
|---|---|---|---|---|---|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

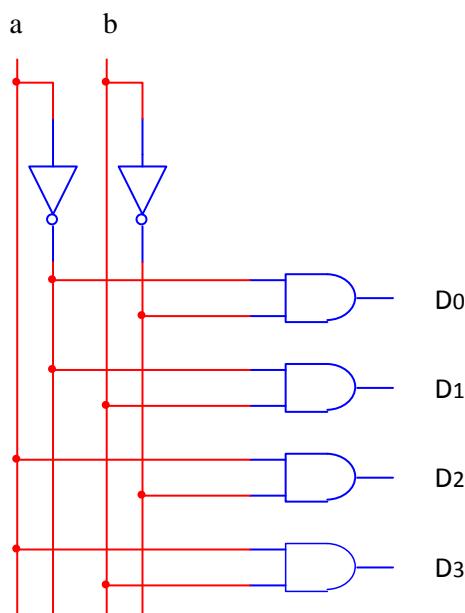The block diagram is given below output 0 is just ($\bar{a}\bar{b}$) , output 1 is ($\bar{a}b$) and output 2 is ($a\bar{b}$) and output 3 is (ab) . Each output corresponds to one of minterms for a two - variable




More decoder also have one or more enable inputs . When such input is active ,the decoder behaves as described . When it is in active , all of the outputs of the decoder are in active . In most system with a sing le enable (not just decoder),that input is active low


| E | a | b | D0 | D1 | D2 | D3 |
|---|---|---|----|----|----|----|
| 1 | x | x | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 |

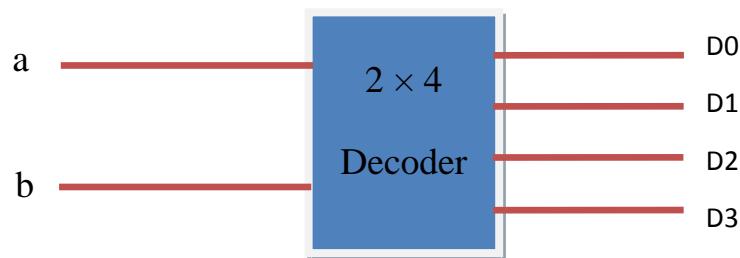

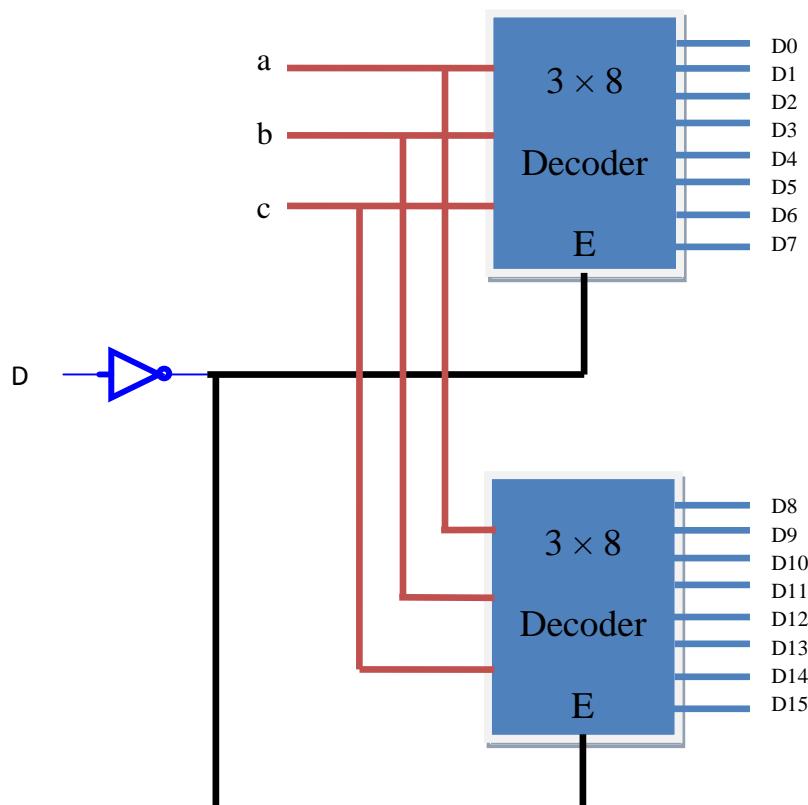Ex / Use two 3×8 decoder with enable input to form a 4 - bit to 16 line decoders



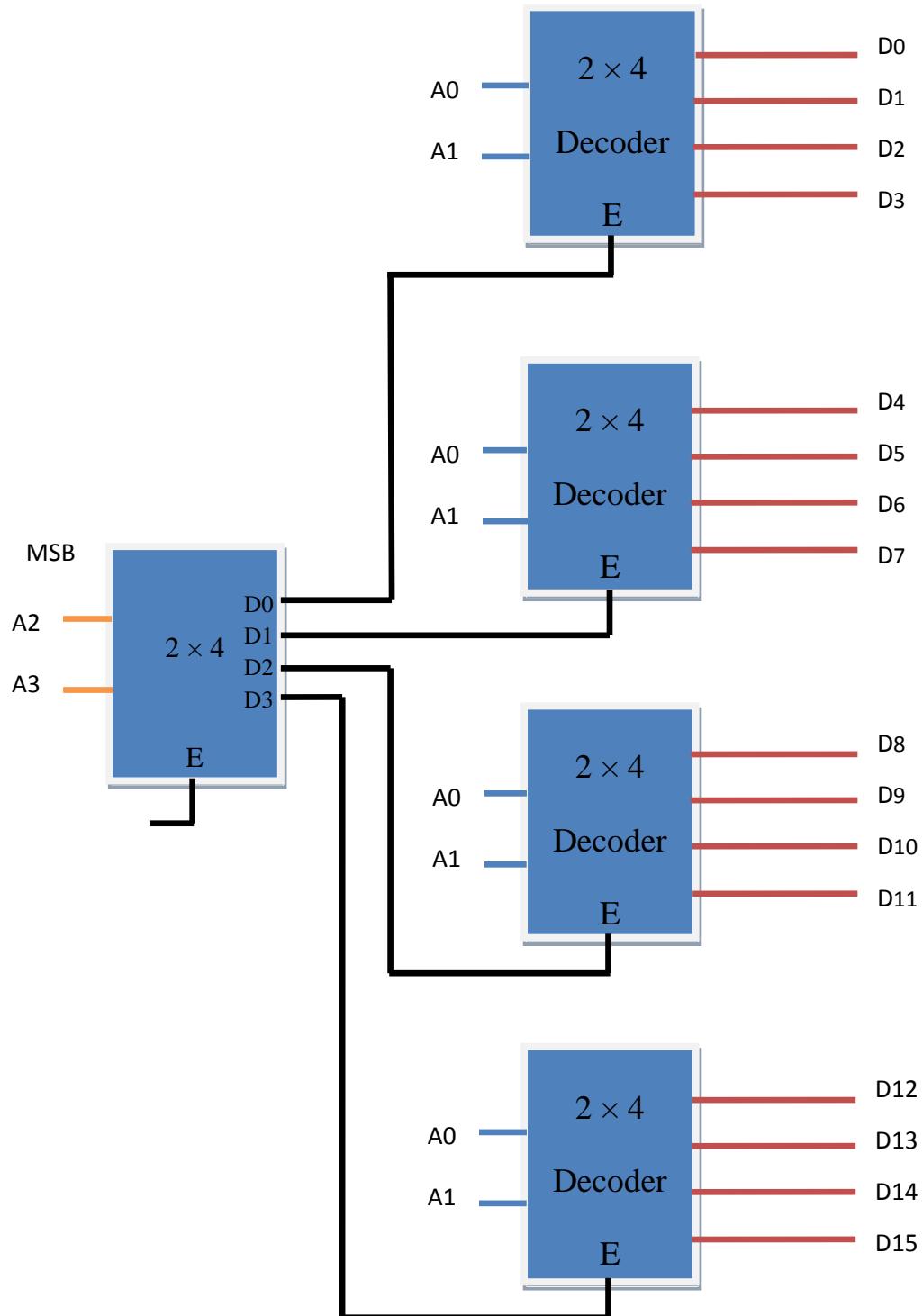Ex / Construct 4 - to - 16 decoder with an enable input using five 2 - to - 4 line decoder with enable inputs.



Ex / A combinational circuit is defined by the following three Boolean functions.

$$F1 = \overline{x+y} + xyz$$

$$F2 = (\overline{x+y}) + \overline{xyz}$$


$$F3 = (\overline{x+y}) + xyz$$

sol /

$$F1 = \overline{xy} + xy\bar{z}$$

$$F2 = \overline{xy} + \overline{x}yz$$

$$F3 = \overline{xy} + xyz$$

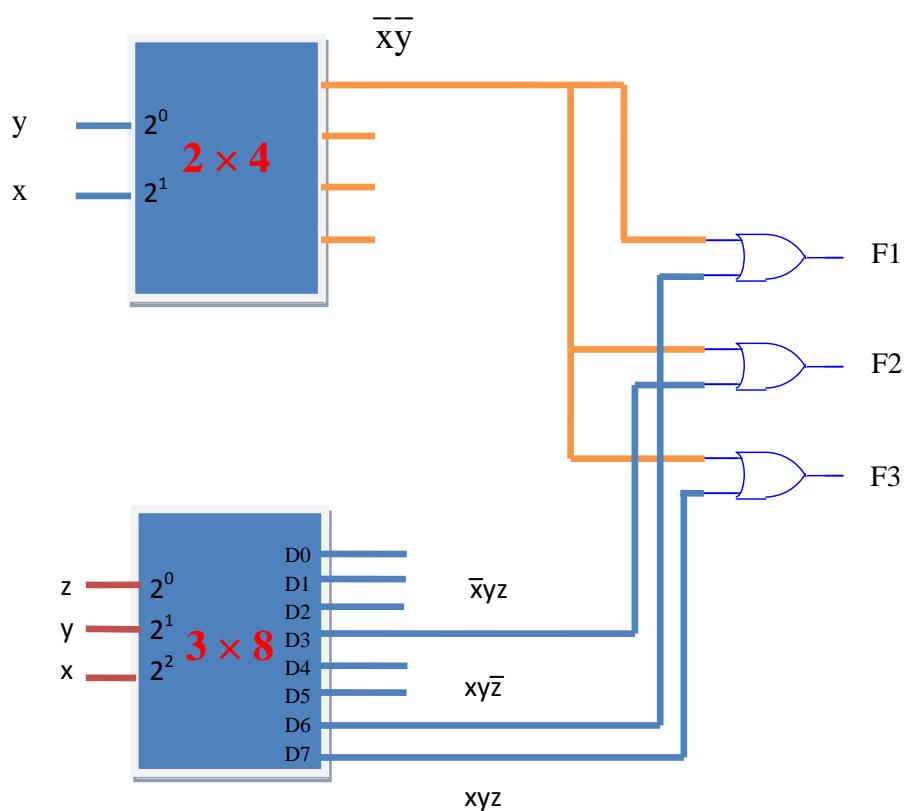

SEVEN - SEGMENT DECODERS:

Figure A , shows a seven segment indicator , i.e , seven LEDs labeled a through g . By forward - biasing different LEDs , we can display the digit 0 through 9 (see figure B) For instance to display a 0, we need to light up segments a,b,c,d,e and f . To light up a 5, We need segments a,b,c,d,f and g.

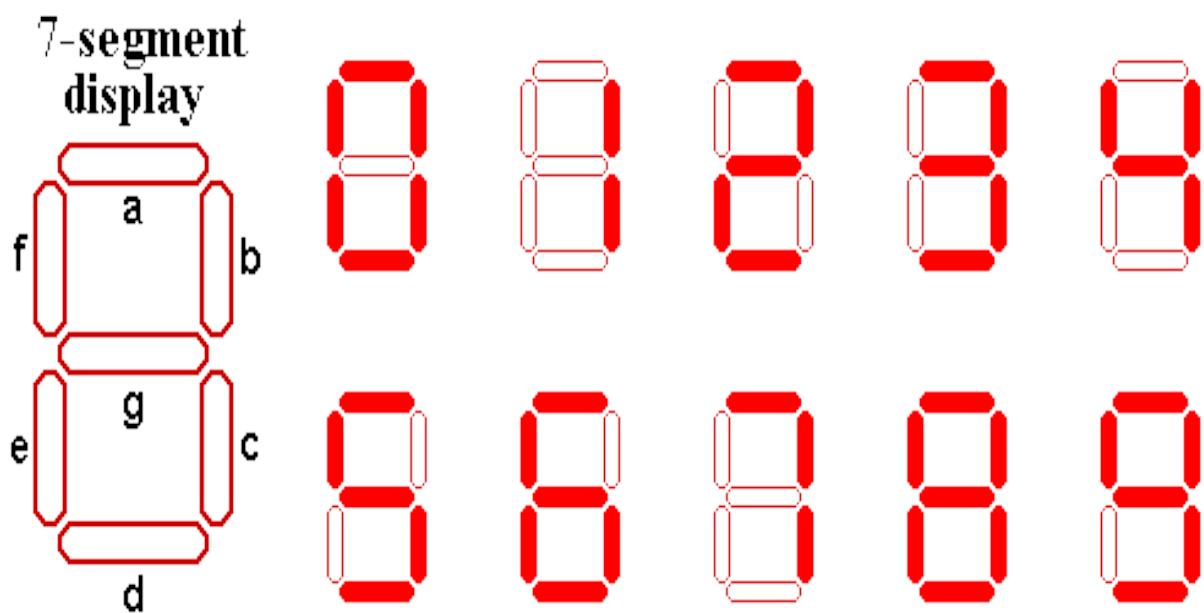





Figure A

Figure B

ENCODER

An Encoder is a digital circuit that performs the inverse operation of a decoder . An Encoder has (2^n) (or fewer) input lines and (n) output lines . The output lines generate binary code corresponding to the input value .

| Input | | | | | | | | Output | | |
|-------|----|----|----|----|----|----|----|--------|---|---|
| D0 | D1 | D2 | D3 | D4 | D5 | D6 | D7 | A | B | C |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

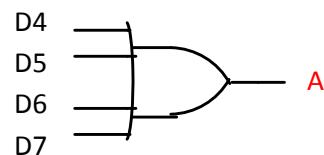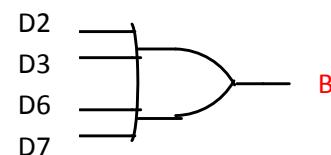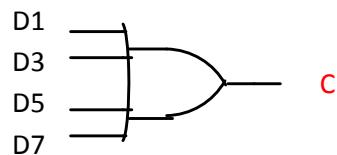

NOTE : Since n Input decoder generates all the minterms of n variables , or generates all the maxterms, function can be realized by ORing selected minterms or ANDing selected maxterms .